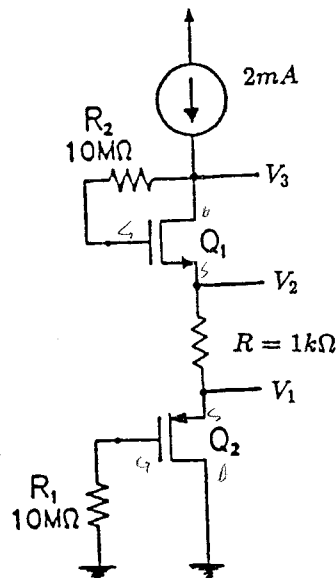


Course	Number	Section	
Electronics II	ELEC 312	U and W	
Examination	Date	Time	# of pages
Final	April 1996	3 Hours	6
Instructor(s)			
Drs. M.B. Gawargy and H.R. Mehrvar			
Materials allowed:	<input type="checkbox"/> No	<input checked="" type="checkbox"/> Yes (Please specify)	
Calculators allowed:	<input type="checkbox"/> No	<input checked="" type="checkbox"/> Yes	
Students are allowed to use pocket-sized electronic calculators only. Students are allowed one double-sided, 8-1/2" x 11" crib sheet.			
Special Instructions:			
Attempt all six (6) questions. All questions carry equal weight. Students are required to return question paper with exam booklet(s). Your answers must be logical, reasoned, concise, and neatly organized.			

- For the MOS transistors shown in Figure 1, $|v_t| = 1 \text{ v}$, $k = 0.5 \text{ mA/v}^2$ and $\lambda = 0$.
 - Find v_1 , v_2 , and v_3 and modes of operations of Q_1 and Q_2 .
 - Find g_{m1} and g_{m2} .

Figure 1



2. Consider the circuit shown in Figure 2.

- (a) Draw the small signal equivalent circuit.
- (b) Find v_o/v_i in terms of circuit parameters, g_{m1} , g_{m2} , r_{o1} , and r_{o2} .

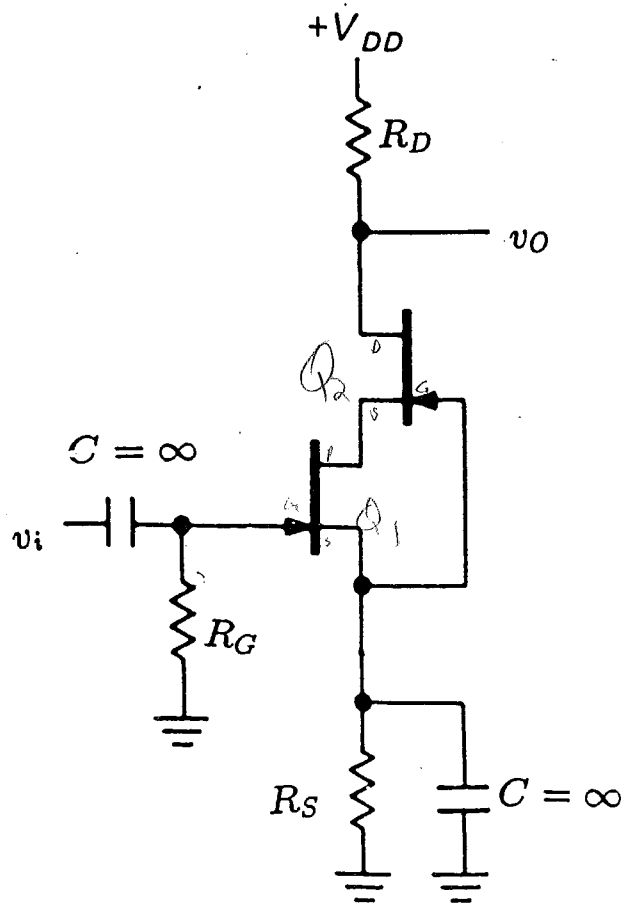


Figure 2

3. BJTs in the differential amplifier shown in Figure 3 have $\beta = 100$, $V_{BE} = 0.7$ V and $r_o = \infty$. Find

- The current in the current source (I).
- r_{e1} and r_{e2} .
- The differential gain v_o/v_d .
- The input resistance R_{id} .
- The range of allowable common mode input.

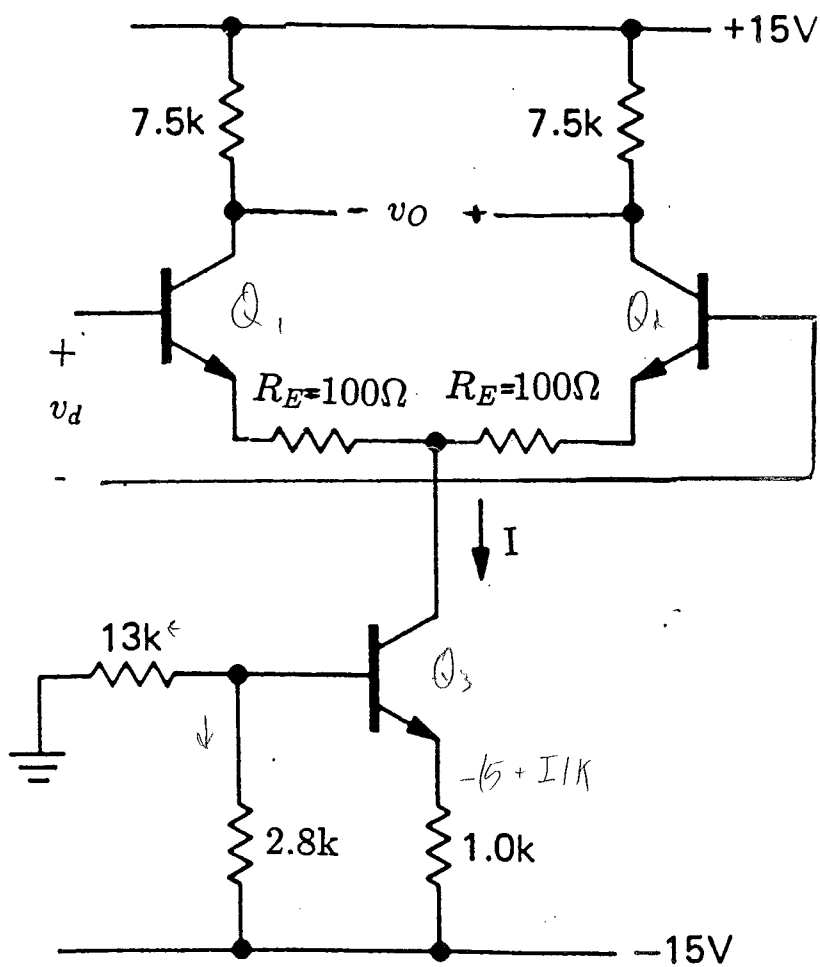


Figure 3

4. Figure 4 shows a Wilson current mirror which uses identical transistors Q_1 , Q_2 and Q_3 . Assume $\beta = 100$ and $I_{E1} = 0.25\text{mA}$, $V_A = 100$ volts.
- (a) Calculate r_e , r_o and g_m .
 - (b) Draw the equivalent circuit for the current mirror. Use the hybrid π models for Q_2 and Q_3 and replace Q_1 with its incremental resistance r_e .
 - (c) Calculate the output resistance of the current mirror seen from the collector of Q_3 .

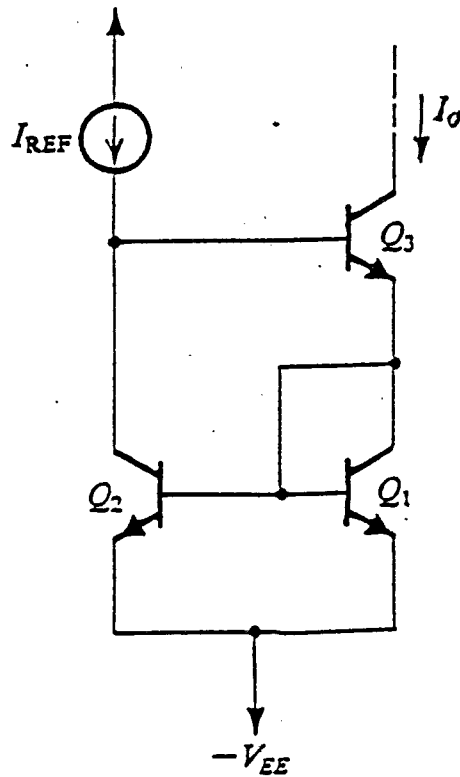


Figure 4

5. Figure 5 shows the high-frequency equivalent circuit of a FET amplifier.
- (a) Derive an expression for the mid-frequency voltage gain (set C_{gs} and C_{gd} to zero).
 - (b) Use open circuit time constant method to derive expressions for R_{gs} and R_{gd} .
 - (c) Let $R = 100\text{k}\Omega$, $g_m = 4\text{mA/V}$, $R_L = 5\text{k}\Omega$, $R_S = 100\Omega$, and $C_{gd} = C_{gs} = 1\text{pF}$. Find the mid-frequency gain and the upper 3-dB ω_H .

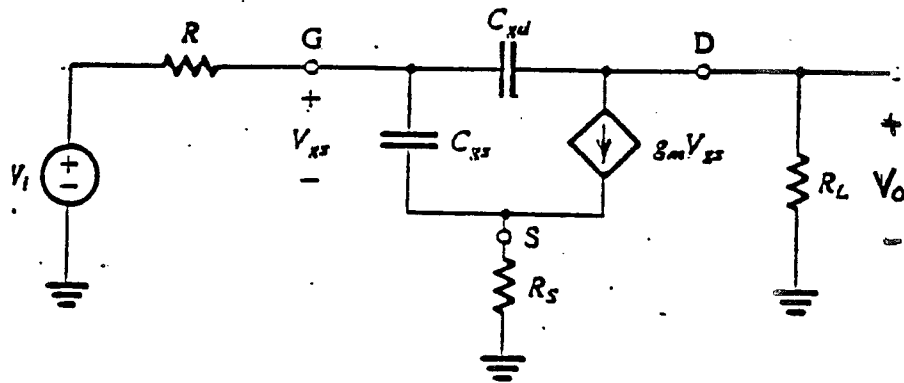


Figure 5

6. Assume that in the circuit of Figure 6 the BJT is operating in the active mode.
- (a) State the type of feedback topology that has been employed in this circuit. Draw the feedback circuit, the A circuit, and the β circuit with all their components expressed in terms of those of the given circuit.
 - (b) Derive expressions for A , R_i , R_o , and β .
 - (c) Derive expressions for $A_f = v_o/v_s$, R_{if} , and R_{of} .
 - (d) Derive expressions for R_{in} and R_{out} , using feedback method.

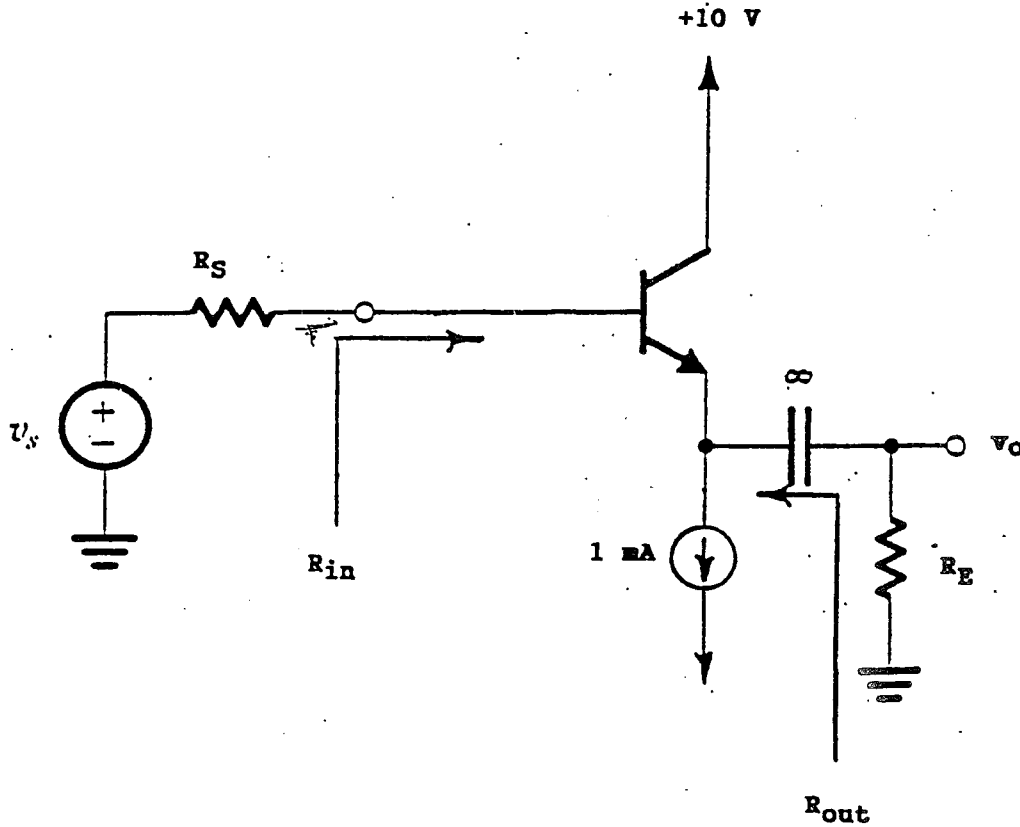


Figure 6

CONCORDIA UNIVERSITY
DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING
MIDTERM EXAMINATION
ELECTRONICS II (ELEC 312/4)

Date: Friday, February 21, 1992

Section U: Dr. M.O. Ahmad

Time: 11:45 a.m. - 1:00 p.m.

Section W: Dr. B.B. Bhattacharyya

- Note:**
- (i) This is a closed-book examination
 - (ii) Electronic calculators are allowed
 - (iii) Attempt all four (4) questions
 - (iv) All questions carry equal weight

Question 1

The NMOS device shown in Figure 1 has the following parameters: $\lambda = 0$, $K = 1 \text{ mA} / \text{V}^2$, and $V_t = 2 \text{ V}$. The resistor $R_{G1} = 4 \text{ k}\Omega$ and the supply voltage $V_{DD} = +5 \text{ V}$. Design the circuit to establish a saturation - region dc operating point of $V_D = 2 \text{ V}$ and $I_D = 1 \text{ mA}$.

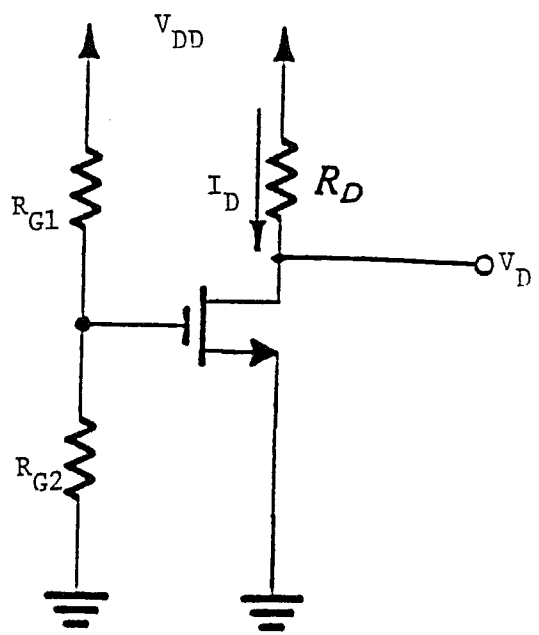


Figure 1

Question 2

The PMOS transistor in the circuit of Figure 2 has $V_t = -1\text{ V}$, $\mu_p C_{ox} = 5\ \mu\text{A}/\text{V}^2$, $L = 10\ \mu\text{m}$, and $\lambda = 0$. Find the values of R and the gate width W in order to establish a drain current of $1\ \text{mA}$ and a voltage $V_D = 2\ \text{V}$.

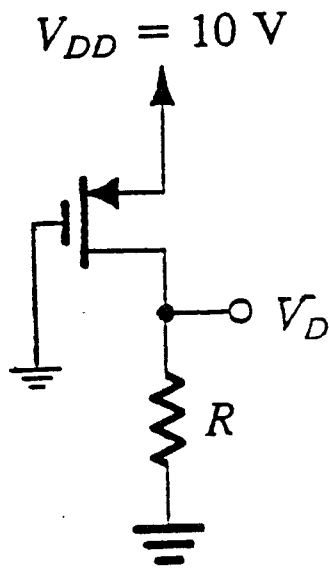


Figure 2

Question 3

For the amplifier circuit shown in Figure 3, assume that the MOSFET is operating in the saturation region and that $\lambda = 0$.

- (a) Derive the expressions for the voltage gains v_{o1}/v_i and v_{o2}/v_i in terms of the circuit components and the FET's small-signal parameters.
- (b) Establish the condition for $v_{o1} = -v_{o2}$.

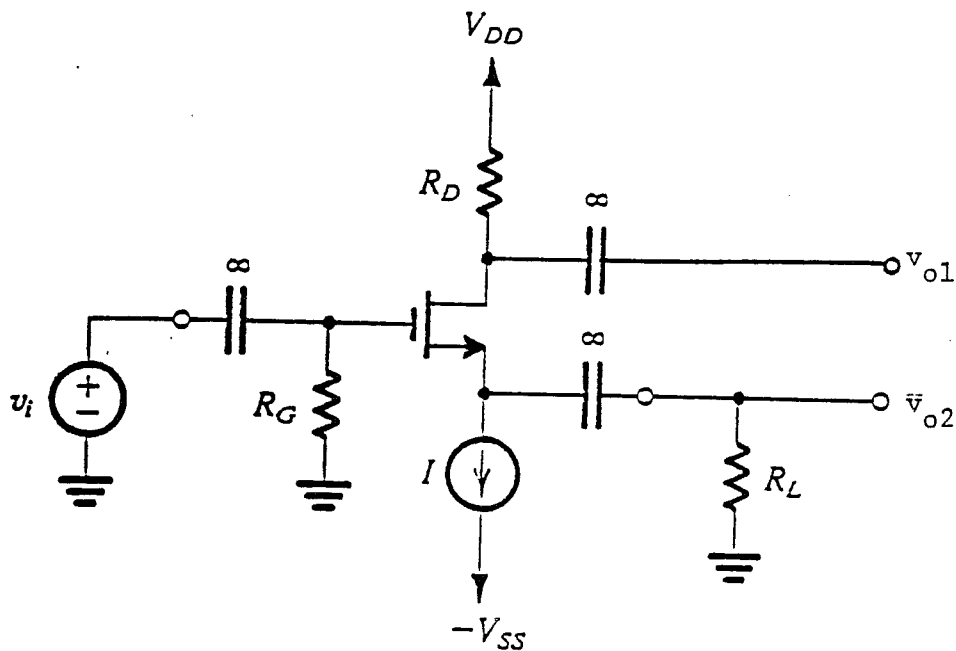


Figure 3

Question 4

The BJTs of the differential amplifier circuit shown in Figure 4 are operating in the active region and have $V_A = \infty$.

- (a) Derive expressions for the dc voltages V_{C1} and V_{C2} and the emitter resistances r_{e1} and r_{e2} .
- (b) Derive expressions for the voltage gain v_o/v_i in terms of the circuit components and the BJTs' small-signal parameters.

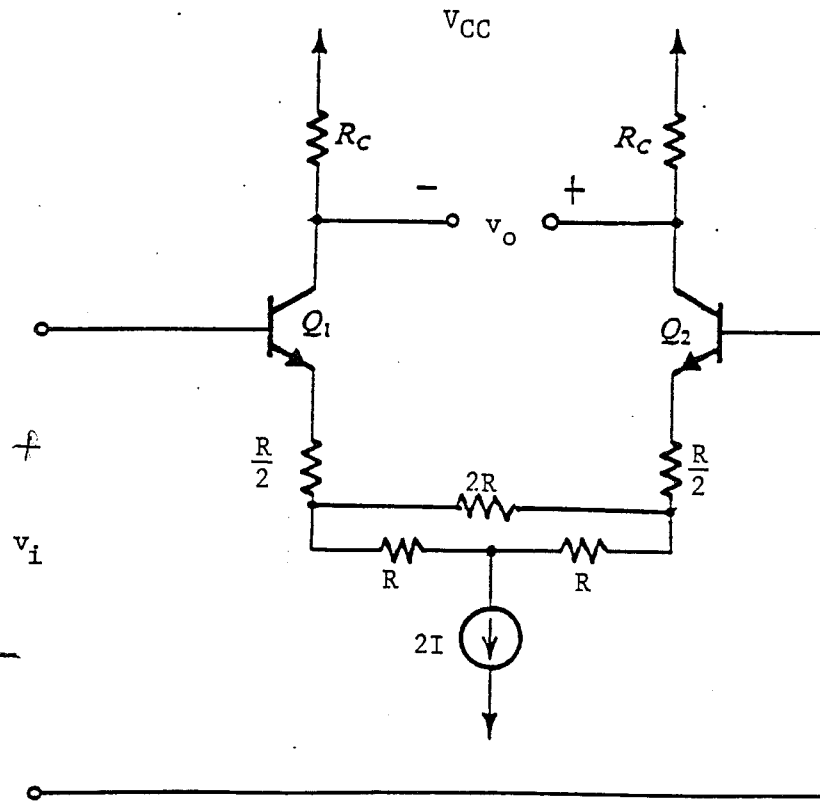


Figure 4

Handwritten notes:

$$r_{e1} = \frac{V_T}{I_{E1}} = \frac{V_T}{I_C} = \frac{V_T}{\beta I_B}$$

$$I_C = \beta I_B$$

Handwritten notes:

$$r_{e2} = \frac{V_T}{I_{E2}} = \frac{V_T}{I_C}$$