

INDUSTRIAL ELECTRONICS MECH 372/2 Section X

Mid-Term #2

Tuesday November 21, 2000

Answer All 3 Questions


Question #1 (a=4, b=1, c=1, d=1, e=2, f=1, g=2, h=2 →→→ 14 marks)

Note: *If formulas are ONLY stated, no marks will be given.
All formulas MUST be derived from circuit analysis. Show all steps in your analysis.*

For the circuit shown below, the following h parameters are given:
 $h_{ie} = 1.4 \text{ k}\Omega$, $h_{fe} = 100$, $h_{oe} = 125 \mu\text{S}$, $h_{re} = \text{neglect}$

- Simplify the circuit below and draw the circuit for DC-analysis.
• Find the quiescent point of the transistor given that $V_{CC} = 20 \text{ V}$ and $\beta = h_{fe} = 100$.
• Assume that the transistor has a diode cut-in voltage $V_{\gamma} = 0.6 \text{ V}$.
- Draw the AC equivalent circuit, using h parameters.
- Derive the expression for the input resistance R_{in} and calculate the numerical value.
- Derive the expression for the output resistance R_o as seen by the load R_L , and calculate the numerical value. **Do not neglect h_{oe} .**
- Derive the open circuit voltage gain μ and calculate the numerical value. **Do not neglect h_{oe} .**
- Using the results from parts (c), (d) and (e), draw the equivalent circuit model of the voltage amplifier.
- Derive the actual voltage gain $A_V = v_L/v_S$ and calculate the numerical value.
- Derive the current gain $A_I = I_L/I_S$ and calculate the numerical value.

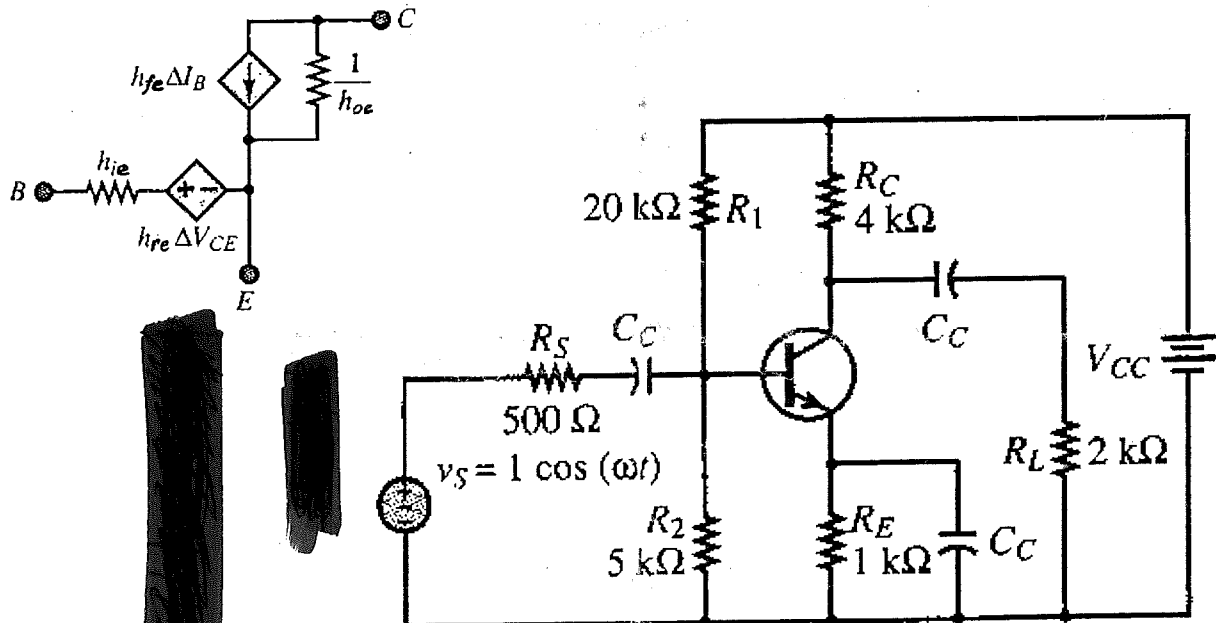Information: The h -parameter small-signal model for BJT is given as:



Question #2 (8 marks)


The figure below shows two transistors operating as a switch, which are connected as two inverters in series, where:

$$R_{1C} = R_{2C} = 10\text{ k}\Omega \text{ and } R_{1B} = R_{2B} = 27\text{ k}\Omega$$

- Find v_B , v_{out} and the (*clearly explain*) state of transistor Q_1 when v_{in} is low.
- Find v_B , v_{out} and the (*clearly explain*) state of transistor Q_1 when v_{in} is high.

NOTE:

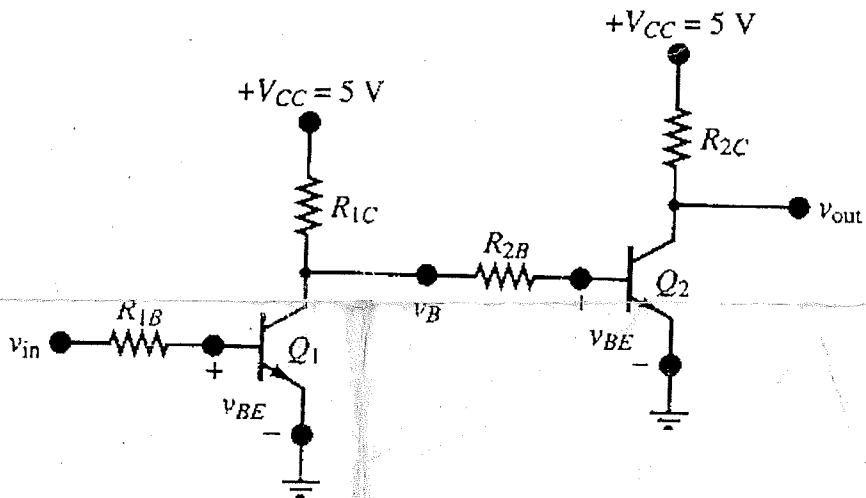
- All assumptions must be stated clearly and with supporting proof.
- Show all relevant equations.
- No marks will be given for numbers simply stated without supporting assumptions or calculations.



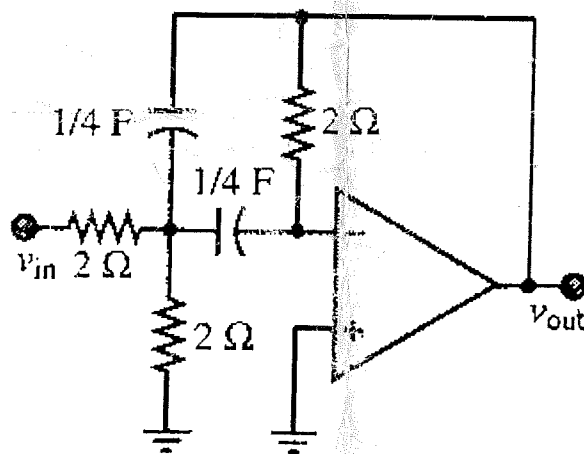Question #3 (8 marks)

Derive the transfer function for the circuit given below.

You must provide mathematical steps and explain any assumptions taken.



669-2162
Karin Cell.